

الاسم:
الرقم:

مسابقة في مادة الفيزياء
المدة: ساعة ونصف


This exam is formed of three obligatory exercises in three pages.
The use of non-programmable calculator is recommended.

Exercise 1 (7 pts)

Mechanical oscillator

A mechanical oscillator is constituted of a block (S) of mass M and a spring of negligible mass and force constant k.

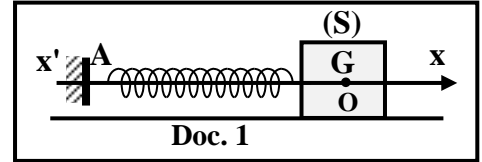The spring, placed horizontally, is connected from one of its extremities to a fixed support A. (S) is attached to the other extremity of the spring and it may slide without friction on a horizontal surface (Doc. 1).



The aim of this exercise is to determine the values of M and k.

At equilibrium, the center of mass G of (S) coincides with the origin O of the x-axis.


(S) is shifted from its equilibrium position in the positive direction and then released without initial velocity at the instant $t_0 = 0$. Thus, (S) performs mechanical oscillations. At an instant t, the abscissa of G is $x = \overline{OG}$ and the algebraic value of its velocity is $v = x' = \frac{dx}{dt}$.

The horizontal plane containing G is considered as a reference level for gravitational potential energy.

- 1) Write, at an instant t, the expression of the mechanical energy ME of the system (Oscillator, Earth) in terms of x, M, k and v.
- 2) Establish the second order differential equation in x that governs the motion of G.
- 3) Deduce that the expression of the proper (natural) period of the oscillations is $T_1 = 2\pi\sqrt{\frac{M}{k}}$.
- 4) An appropriate device traces x as a function of time (Doc. 2).

Referring to document 2, indicate:

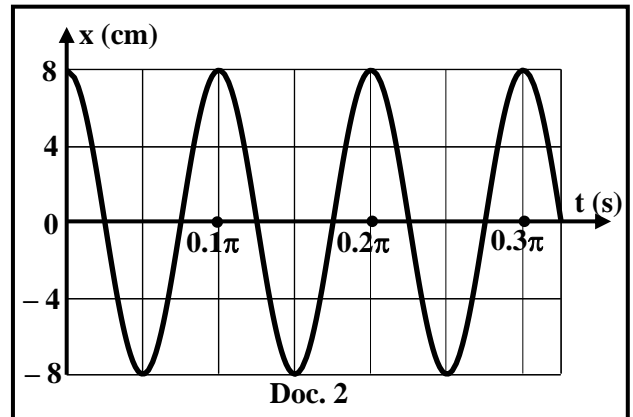- 4.1) the type of oscillations of G;
- 4.2) the amplitude X_m of the oscillations;
- 4.3) the value of T_1 .
- 5) The same experiment is repeated by putting on (S) an object, considered as a particle, of mass $m = 50$ g. The duration of 10 oscillations becomes $\Delta t = 3.67$ s.
 - 5.1) Write the expression of the new proper (natural) period T_2 of the oscillations in terms of k, M and m.
 - 5.2) Using the expressions of T_1 and T_2 , show that $k = \frac{4\pi^2 m}{T_2^2 - T_1^2}$.
 - 5.3) Determine the values of k and M.



Exercise 2 (7 pts)

Charging and discharging a capacitor

The aim of this exercise is to study the charging and the discharging of a capacitor.

For this purpose, we set up the circuit of document 3 that includes:

- an ideal battery of electromotive force $E = 10 \text{ V}$;
- two resistors of resistances $R_1 = R_2 = 4 \text{ k}\Omega$;
- a capacitor of capacitance C ;
- a switch K .

1) Charging the capacitor

The switch K is initially at position (0) and the capacitor is uncharged.

At the instant $t_0 = 0$, K is turned to position (1) and the charging process of the capacitor starts.

At an instant t , plate B of the capacitor carries a charge q and the circuit carries a current i .

An appropriate device allows us to display the voltage $u_{AB} = u_{R_1}$ across the resistor and the voltage $u_{BD} = u_C$ across the capacitor.

Curves (a) and (b) of document 4 show these voltages as functions of time.

1.1) Curve (a) represents u_{R_1} and curve (b) represents u_C . Justify.

1.2) The time constant of this circuit is given by $\tau_1 = R_1 C$.

1.2.1) Using document 4, determine the value of τ_1 .

1.2.2) Deduce the value of C .

1.3) Calculate the time « t_1 » needed by the capacitor to practically become completely charged.

2) Discharging the capacitor

The capacitor is completely charged. At an instant taken as a new initial time $t_0 = 0$, the switch K is turned to position (2), and the capacitor starts discharging through the resistors of resistances R_1 and R_2 . At an instant t the circuit carries a current i (Doc. 5).

2.1) Show, using the law of addition of voltages, that the differential equation which governs u_C is:

$$RC \frac{du_C}{dt} + u_C = 0 \quad \text{where } R = R_1 + R_2.$$




2.2) The solution of this differential equation is of the form: $u_C = E e^{\frac{-t}{\tau_2}}$ where τ_2 is the time constant of the circuit of document 5.

Determine the expression of τ_2 in terms of R and C .

2.3) Verify that the time needed by the capacitor to practically become completely discharged is $t_2 = 5 \tau_2$.

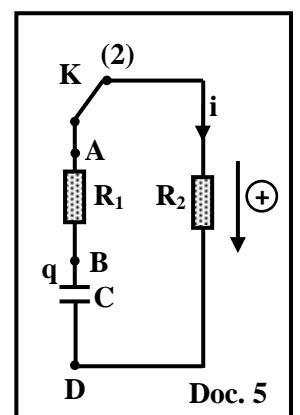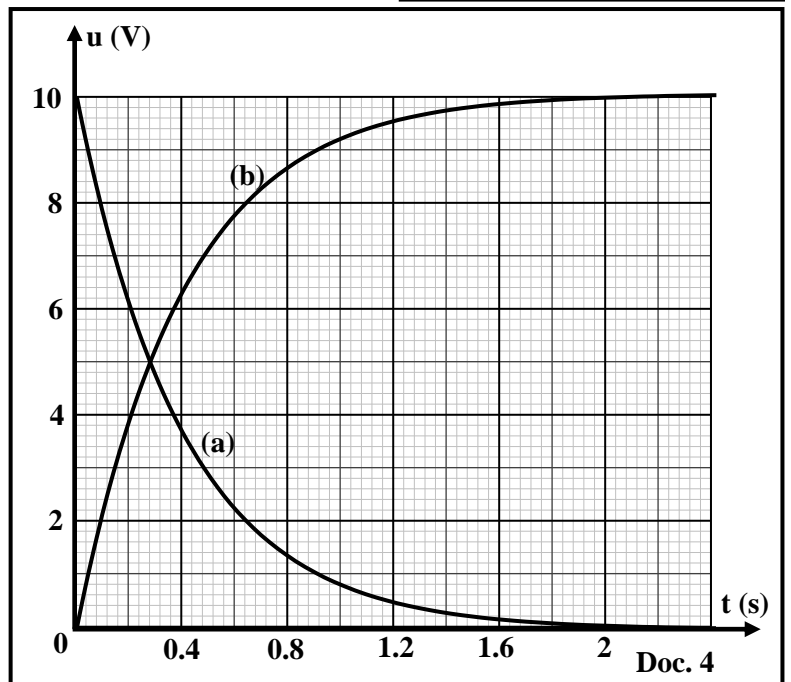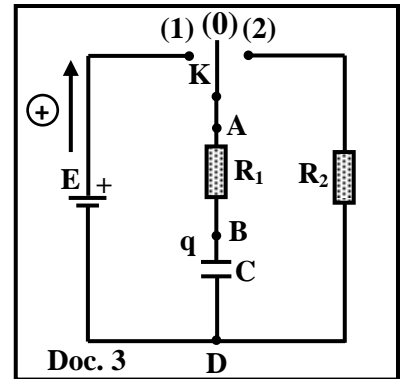3) Duration of charging and discharging the capacitor

Show, without calculation, that « t_2 » is greater than « t_1 ».



Exercise 3 (6 pts)

Characteristics of a coil

In order to determine the inductance L and the resistance r of a coil, we connect it in series with a resistor of resistance $R = 30 \Omega$ across a function generator (G) providing an alternating sinusoidal voltage of angular frequency ω .

The circuit thus carries an alternating sinusoidal current of expression $i = I_m \sin(\omega t)$ (Doc. 6).

An oscilloscope allows us to display the voltage $u_{AB} = u_R$ across the resistor and the voltage $u_{BC} = u_L$ across the coil.

The obtained waveforms are shown in document 7.

The adjustments of the oscilloscope are:

- vertical sensitivity for both channels: $S_v = 2 \text{ V/div}$;
- horizontal sensitivity: $S_h = 0.4 \text{ ms/div}$.

1) The voltage u_R represents the image of i . Why?

2) Referring to document 7, specify which of the curves, (a) or (b), leads the other.

3) Deduce that curve (a) corresponds to u_{AB} .

4) Using document 7, determine:

4.1) the angular frequency ω ;

4.2) the maximum value I_m of i ;

4.3) the phase difference φ between u_L and i .

5) Prove that $u_L = 6.8 \sin(\omega t + 0.4\pi)$ (SI).



6) Knowing that the voltage across the coil is given

by $u_L = r i + L \frac{di}{dt}$, write the expression of u_L in

terms of r , L , ω and t .

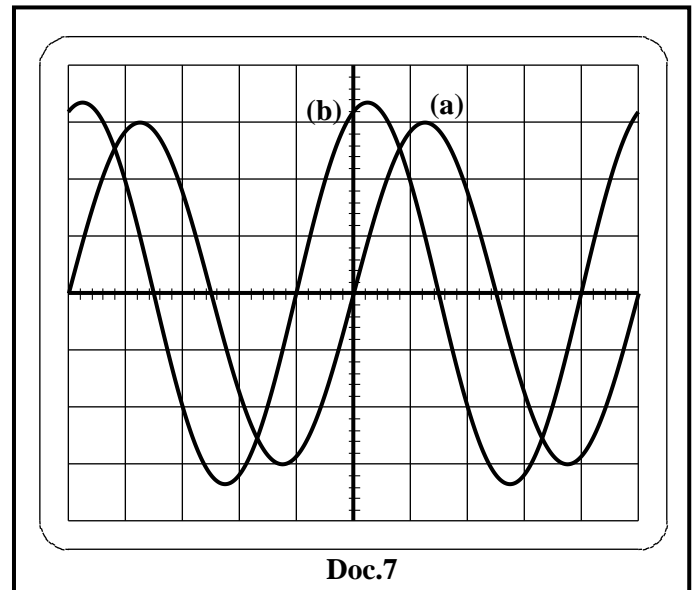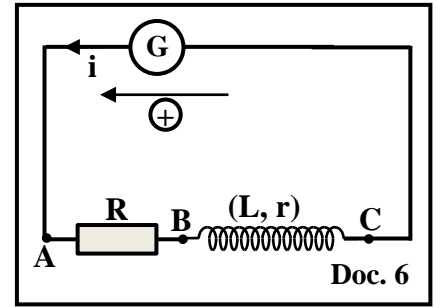7) Using the two expressions of u_L found in parts 5

and 6 and by giving « ωt » two particular values, determine the values of L and r .



الاسم:
الرقم:

مسابقة في مادة الفيزياء
المدة: ساعة ونصف

Exercise 1 (7 pts)

Mechanical oscillator

Part	Answer	Note
1	$ME = KE + EPE = \frac{1}{2} M v^2 + \frac{1}{2} kx^2$	0.5
2	The sum of the works done by the non-conservative forces is zero, then the mechanical energy is conserved. (Or: Friction is neglected, then the mechanical energy is conserved). $ME = \text{constant}$, then $\frac{dME}{dt} = 0$, so $M v v' + k x x' = 0$, but $v = x'$ and $v' = x''$, hence $v (M x'' + k x) = 0$ $v = 0$ is rejected , then $x'' + \frac{k}{M} x = 0$	1
3	The differential equation is of the form: $x'' + \omega_0^2 x = 0$, with $\omega_0 = \sqrt{\frac{k}{M}}$ $T_1 = \frac{2\pi}{\omega_0}$; therefore, $T_1 = 2\pi\sqrt{\frac{M}{k}}$	1
4	4.1 Free undamped mechanical oscillations	0.5
	4.2 $X_m = 8 \text{ cm}$	0.5
	4.3 From the curve: $T_1 = 0.1 \pi \text{ s} = 0.314 \text{ s}$	0.5
5	5.1 $T_2 = 2\pi\sqrt{\frac{M+m}{k}}$	0.5
	5.2 $T_1^2 = 4\pi^2 \frac{M}{k}$ and $T_2^2 = 4\pi^2 \left(\frac{M+m}{k}\right)$ $T_2^2 - T_1^2 = 4\pi^2 \left(\frac{M+m}{k} - \frac{M}{k}\right) = \frac{4\pi^2 m}{k}$, so $k = \frac{4\pi^2 m}{(T_2^2 - T_1^2)}$	1
	5.3 $T_2 = \frac{3.67}{10} = 0.367 \text{ s}$ $k = \frac{4\pi^2 \times 0.05}{0.367^2 - 0.314^2}$, then $k = 54.7 \text{ N/m}$ $T_1^2 = 4\pi^2 \frac{M}{k}$, substituting the value of k into this expression gives: $0.314^2 = 4\pi^2 \frac{M}{54.7}$; therefore, $M = 0.1366 \text{ kg} = 136.6 \text{ g}$	0.5 0.5 0.5

Exercise 2 (7 pts)

Charging and discharging of a capacitor

Part	Answer	Note
1	<p>Curve (a): $u_{AB} = u_{R_1} = R_1 i$; u_{R_1} is directly proportional to the current in the circuit. During the charging process, the current decreases so u_{R_1} decreases. Curve (b) : $u_{BD} = u_C = \frac{q}{C}$; During charging process q increases so u_C increases</p>	<p>0.5 0.5</p>
	<p>At $t = \tau_1$: $u_C = 0.63 E = 6.3 V$ From document 4: $u_C = 6.3 V$ at $t = 0.4 s$, then $\tau_1 = 0.4 s$</p>	1
	<p>$\tau_1 = R_1 C$, so $C = \frac{\tau_1}{R_1} = \frac{0.4}{4000}$, hence $C = 1 \times 10^{-4} F = 100 \mu F$</p>	0.5
	<p>$t_1 = 5\tau_1 = 5 \times 0.4$, then $t_1 = 2 s$</p>	0.5
2	<p>$u_{BD} = u_{BA} + u_{AD}$ $u_C = R_1 i + R_2 i$, then $u_C = (R_2 + R_1) i = R i$ But, $i = - \frac{dq}{dt} = - C \frac{du_C}{dt}$, hence $u_C = - R C \frac{du_C}{dt}$ Therefore, $R C \frac{du_C}{dt} + u_C = 0$</p>	1.5
	<p>$u_C = E e^{-\frac{t}{\tau_2}}$, then $\frac{du_C}{dt} = - \frac{E}{\tau_2} e^{-\frac{t}{\tau_2}}$ Substituting u_C and $\frac{du_C}{dt}$ into the differential equation gives: $R C (- \frac{E}{\tau_2} e^{-\frac{t}{\tau_2}}) + E e^{-\frac{t}{\tau_2}} = 0$, so $E e^{-\frac{t}{\tau_2}} (1 - \frac{R C}{\tau_2}) = 0$ $E e^{-\frac{t}{\tau_2}} = 0$ is rejected, then $1 - \frac{R C}{\tau_2} = 0$, so $\tau_2 = R C$</p>	1.5
	<p>At $t = 5 \tau_2$: $u_C = E e^{-\frac{5\tau_2}{\tau_2}} = E e^{-5} \cong 0$, so the capacitor is practically completely discharged.</p>	0.5
3	<p>$t_1 = 5 R_1 C$ and $t_2 = 5 R C = 5 (R_1 + R_2) C$ $(R_1 + R_2) > R_1$, then $t_2 > t_1$</p>	0.5

Exercise 3 (6 pts)

Characteristics of a coil

Part	Answer	Note
1	$u_R = Ri$, but R is a positive constant , then u_R and i are directly proportional ; therefore, u_R is the image of current.	0.5
2	Curve (b) leads curve (a), since curve (b) becomes maximum before curve (a).	0.5
3	The voltage across the coil u_L leads u_R (or i). Curve (b) leads curve (a), then curve (a) corresponds to $u_R = u_{AB}$.	0.5
4	4.1 $T = 5 \times 0.4 = 2 \text{ ms} = 2 \times 10^{-3} \text{ s}$ $\omega = \frac{2\pi}{T} = \frac{2\pi}{2 \times 10^{-3}}$, hence $\omega = 1000 \pi \text{ rad/s}$	0.25 0.5
	4.2 Curve (a): $U_{R(\max)} = 3 \times 2 = 6 \text{ V}$ $U_{R(\max)} = R \times I_m$, then $I_m = \frac{6}{30} = 0.2 \text{ A}$	0.25 0.5
	4.3 $\varphi = \frac{2\pi d}{D} = \frac{2\pi \times 1}{5}$, then $\varphi = 0.4 \pi \text{ rad}$	0.5
5	From curve (b): $U_{L(\max)} = 3.4 \times 2 = 6.8 \text{ V}$, and u_L leads i by $\varphi = 0.4\pi \text{ rad}$ $u_L = U_{L(\max)} \sin(\omega t + \varphi)$; therefore, $u_L = 6.8 \sin(\omega t + 0.4 \pi)$	0.25 0.25
6	$u_L = r i + L \frac{di}{dt} = r I_m \sin(\omega t) + L I_m \omega \cos(\omega t)$ $u_L = 0.2 r \sin(\omega t) + L (0.2) (1000\pi) \cos(\omega t) = 0.2 r \sin(\omega t) + 200\pi L \cos(\omega t)$ (SI) Or $u_L = 0.2 r \sin(\omega t) + \omega L (0.2) \cos(\omega t)$ (SI)	0.5
7	$6.8 \sin(\omega t + 0.4 \pi) = 0.2 r \sin(\omega t) + 200 \pi L \cos(\omega t)$ For $\omega t = 0$: $6.8 \sin(0.4 \pi) = 0 + 200\pi L$, then $L = 0.01 \text{ H}$ For $\omega t = \frac{\pi}{2} \text{ rad}$: $6.8 \sin(\frac{\pi}{2} + 0.4 \pi) = 0.2 r + 0$, then $r = 10.5 \Omega$	0.75 0.75